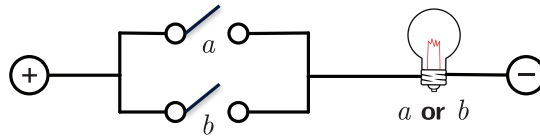


(a)



(b)

Figure 2.1 Simple electrical implementations of an (a) **and** (b) **or** gate.

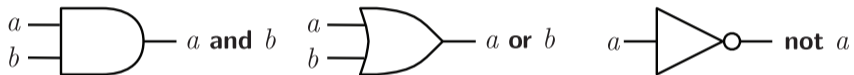


Figure 2.2 Schematic representations of logic gates.